

BHARTIYA VIDYA MANDIR (BVM) COLLEGE OF MGMT. EDUCATION

QUESTION BANK

BCA- II SEM (JU)

202 – COMPUTER ORGANIZATION

Note : All questions carry 2.5 marks.

- Q.1 What is Multiplexer?
- Q.2 What is Flip Flop?
- Q.3 What is Decoder?
- Q.4 What is X-OR Gate?
- Q.5 What is Adder? Explain its .
- Q.6 Explain the 8 to 1 Multiplexer.
- Q.7 What is seven segments Decoder?
- Q.8 What is Encoder?
- Q.9 What is JK Flip Flop?
- Q.10 What is Register?